



# **Preventing the Trip of My Circuit Breaker: Controlling Room Temperature while Brewing Tea**

**Victoria Kovalchuk  
Boston University  
Physical Electronics Lab**


**04/25/2021**

# Basic Idea


- Problem 1: Circuit breaker trips
- Problem 2: Constantly adjusting heater
- Solution:
  - Measure ambient temperature
  - Detect whether kettle is operating
  - Use Microcontroller and relay to turn the heater on/off



# Flowchart

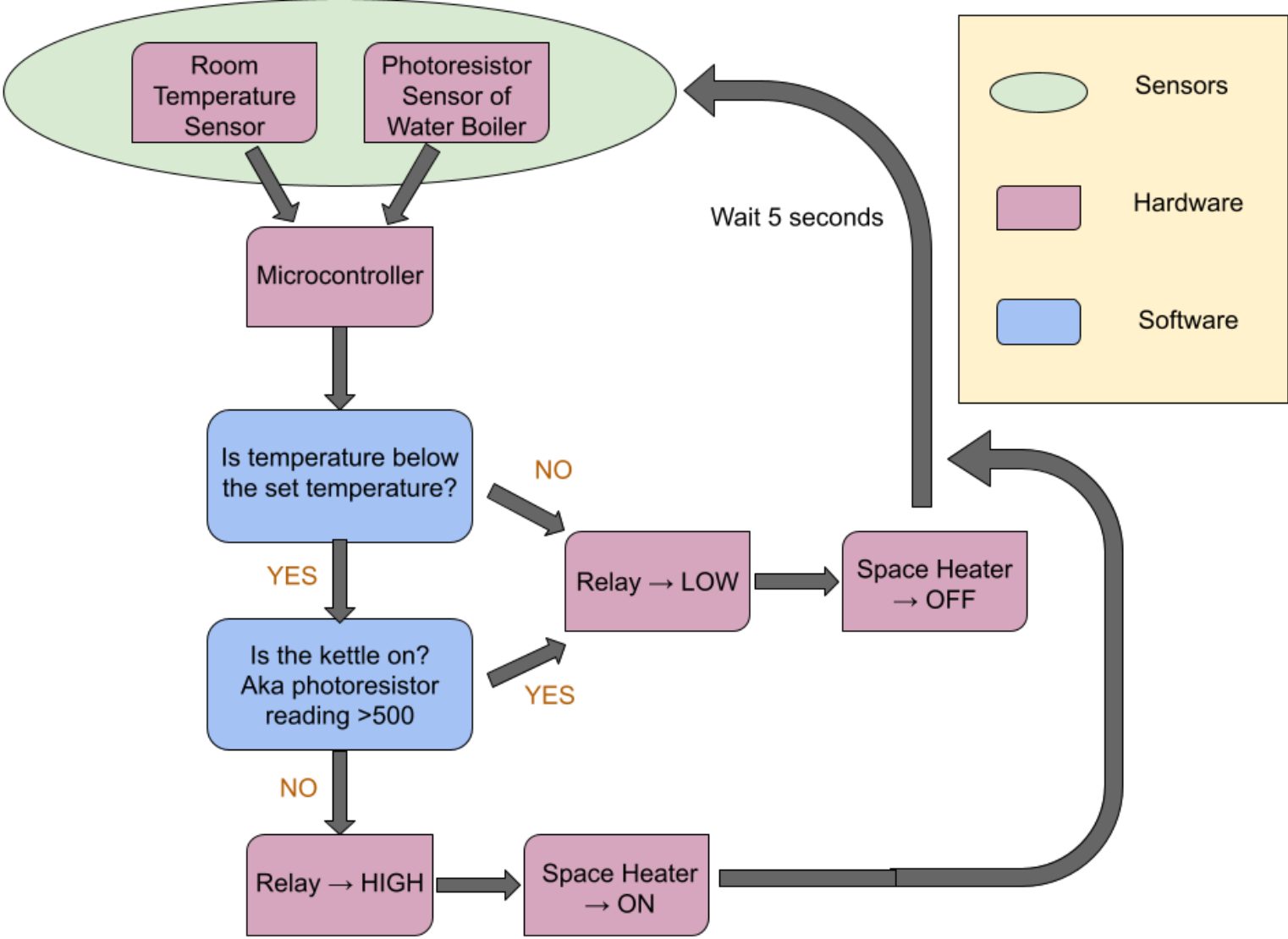

# Electronic Schematic

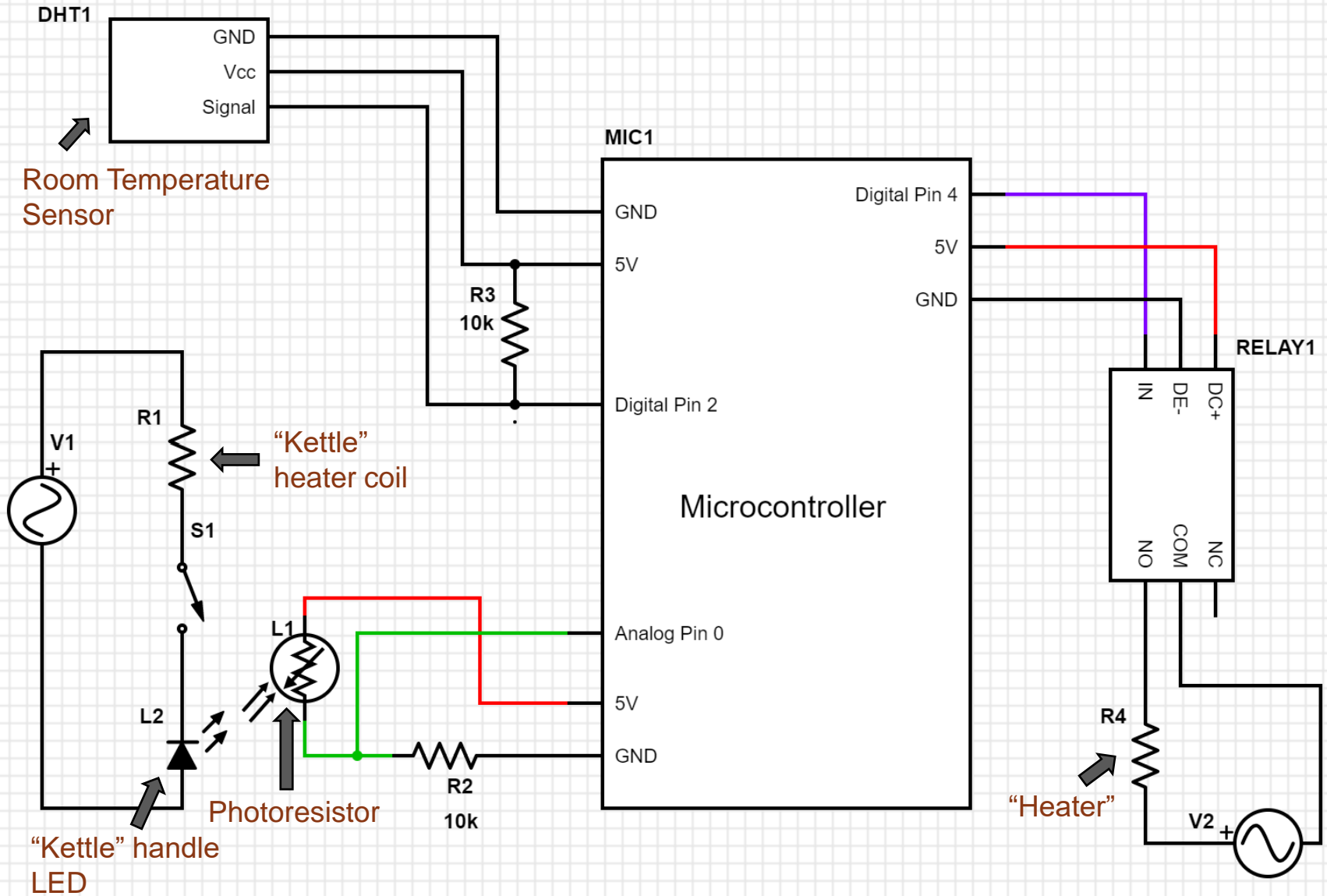




# Putting it Together




Kettle plugged into outlet

Photoresistor attached to kettle light

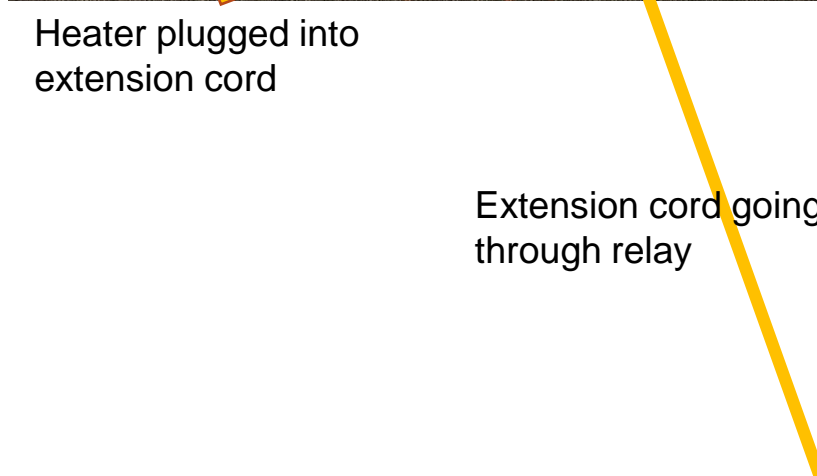

Heater plugged into extension cord

Extension cord going through relay

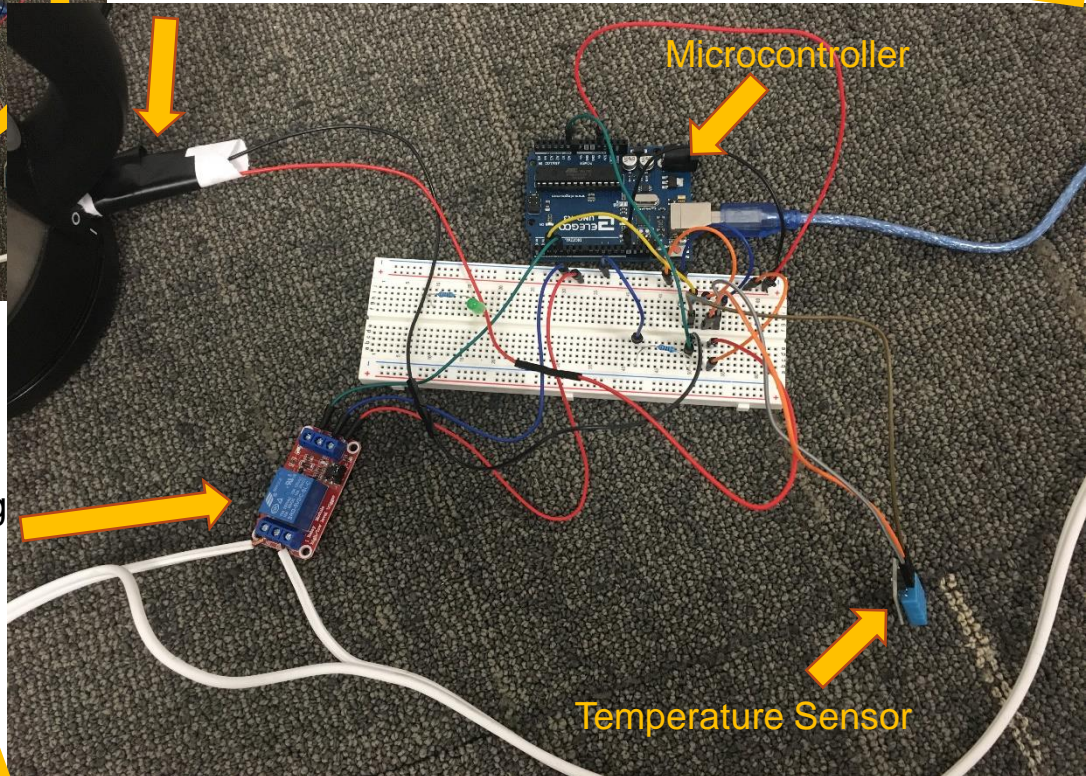

Microcontroller


Temperature Sensor

# Thank you!


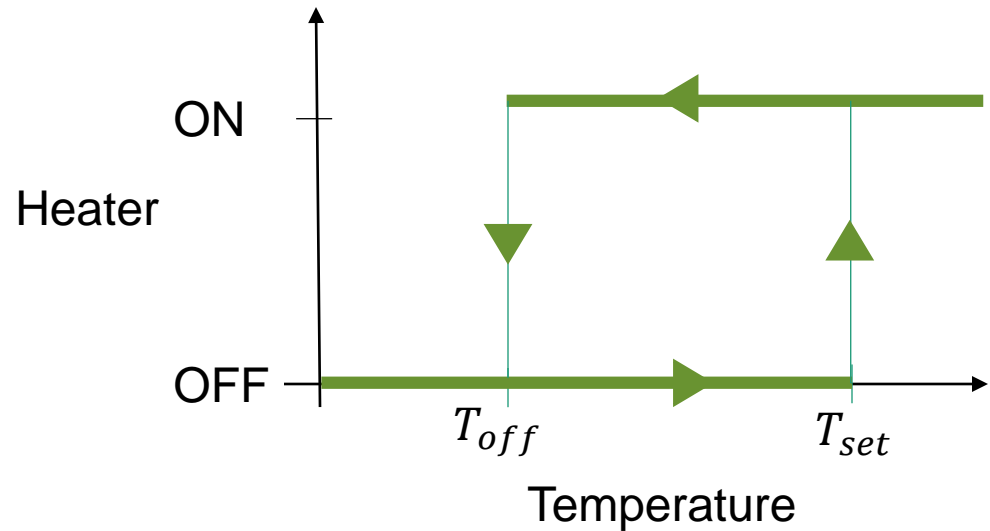
# Hysteresis (Schmitt Trigger)

- Implemented in the code
- Keeps device from continuously turning on/off



# Electronic Schematic

