

$$k = 9.0 \times 10^9 \text{ N m}^2 / \text{C}^2 \quad e = 1.60 \times 10^{-19} \text{ C} \quad \epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2 / \text{N m}^2$$

$$\text{Coulomb's law: } F = k q Q / r^2 \quad (\text{unlike charges attract, like charges repel})$$

$$\text{Electric field from a point charge: } E = k q / r^2 \quad (\text{towards -, away from +})$$

$$\text{Force on a charge in an electric field: } \mathbf{F} = q\mathbf{E}$$

$$\text{Potential energy of two charges: } U = k q Q / r \quad \text{Electric potential: } V = k q / r$$

$$\text{Potential energy of a charge in an electric potential: } U = qV$$

$$\text{Uniform field between two parallel plates a distance } d \text{ apart: } E = V / d$$

$$\text{Accelerating a charge through a potential difference: } qV = \frac{1}{2} mv^2$$

Circuits

$$\text{Capacitance of a parallel-plate capacitor: } C = \kappa \epsilon_0 A / d$$

$$\text{Charge on a capacitor: } Q = CV \quad \text{Energy in a capacitor: } U = \frac{1}{2} CV^2$$

$$\text{Resistance: } R = \rho L / A \quad (\rho = \text{resistivity, } L = \text{length, } A = \text{cross-sectional area})$$

$$\text{Ohm's Law: } V = IR \quad \text{Current: } I = \Delta Q / \Delta t$$

$$\text{Resistors in series: } R = R_1 + R_2 + R_3 + \dots$$

$$\text{Resistors in parallel: } 1/R = 1/R_1 + 1/R_2 + 1/R_3 + \dots$$

$$\text{Electric power: } P = VI = I^2 R = V^2 / R \quad 1 \text{ Watt} = 1 \text{ J / s}$$


PROBLEM 1 – 20 points

A point object with a positive charge $+Q$ is placed on the x-axis at $x = -d$. A second point object of unknown charge is placed at an unknown location on either the x-axis or the y-axis.

The potential energy associated with the charges is $U = +\frac{2kQ^2}{d}$

The potential at the origin due to the charges is $V = +\frac{4kQ}{d}$

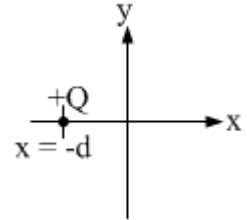The net electric field at the origin due to the two charges points in the negative x direction. Assume the electric potential is zero at infinity.



[8 points] (a) Before solving for the unknown charge and location answer these questions.

(i) What is the sign of the unknown charge?

☐ positive ☐ negative ☐ can not be determined

How do you know?

(ii) Where is the unknown charge located?

☐ positive x-axis ☐ negative x-axis ☐ positive y-axis ☐ negative y-axis


How do you know?

[8 points] (b) Determine the value (sign and magnitude) of the unknown charge and state its location.

[4 points] (c) What is the magnitude of the electric field at the origin?

PROBLEM 2. [20 points] – Light bulbs

The bulbs in the circuit are identical.

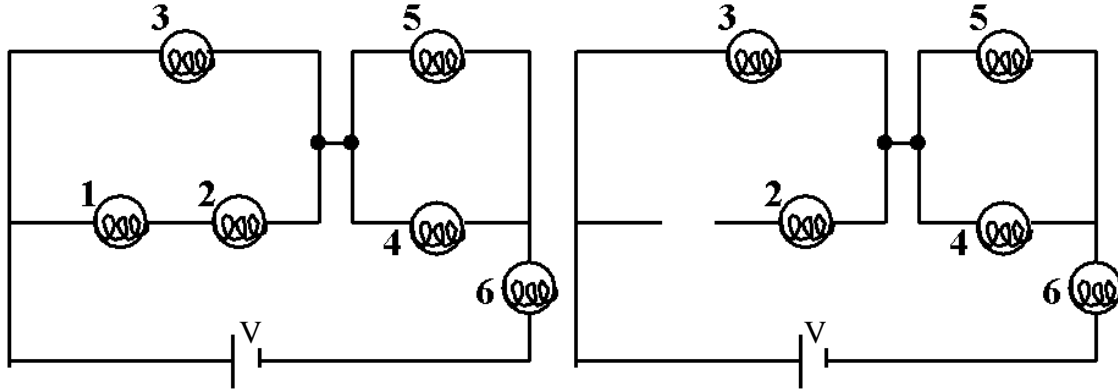

- (1) [6 points] In the circuit on the left, rank bulbs 1-6 in order of **decreasing** brightness. Briefly explain your answers.

- (2) [6 points] If each bulb has a resistance of 12 ohms, what is the equivalent resistance of the circuit on the left?

- (3) [8 points] When bulb 1 is removed, leaving a break in the circuit....

a) The brightness of bulb 3 _____

☐ increases ☐ decreases ☐ stays the same

Briefly explain your answer:

b) The brightness of bulb 6 _____

☐ increases ☐ decreases ☐ stays the same

Briefly explain your answer:


PROBLEM 3 – 20 points

Three resistors are connected as shown in a circuit with a 12 volt battery. The resistances are:

For resistor A, $R_A = 4\ \Omega$

For resistor B, $R_B = 3\ \Omega$

For resistor C, R_C is an unknown value

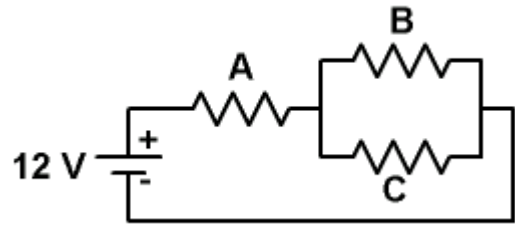

[3 points] (a) Which resistor has the most current passing through it?

☐ A ☐ B ☐ C ☐ It depends on the value of R_C

Briefly justify your answer:

[5 points] (b) Rank the resistors based on the potential difference across them, from largest to smallest.

☐ $A > B > C$ ☐ $A > B = C$ ☐ $B > C > A$ ☐ $B = C > A$
☐ It depends on the value of R_C

Briefly justify your answer:

[8 points] (c) If R_C , the resistance of resistor C, is increased, what happens to the currents through the different elements in the circuit?

i) The current through the battery: ☐ increases ☐ decreases ☐ stays the same

ii) The current through A: ☐ increases ☐ decreases ☐ stays the same

iii) The current through B: ☐ increases ☐ decreases ☐ stays the same

iv) The current through C: ☐ increases ☐ decreases ☐ stays the same

[4 points] (d) If the current through the battery is 2.0 amps, what is R_C , the resistance of resistor C?