

Problem 1.

What you will need: Potential energy of interaction of 2 point charges: $U = \frac{kq_1q_2}{d}$,

Potential, produced by a point charge: $V = \frac{kq}{r}$, electric field due to a point charge:

$$E = \frac{kq}{r^2}$$

a) Since potential energy of interaction of the 2 charges is positive then $q_1q_2 > 0$. Thus, since q_1 is positive then q_2 is also positive. If the second charge was located on the y-axis the vertical component of the total electric field at the origin would not be zero. So, the second charge is somewhere on x-axis. The field at the origin points towards the first charge. This is only possible if the second positive charge is placed on the positive x-axis.

b) Say the distance from the second charge q_2 to the origin is d_2 . Taking into account the conclusions we made in part a) we can express the potential energy of interaction and the potential at the origin as follows:

$$U = \frac{kq_1q_2}{d + d_2} = \frac{2kq^2}{d}$$

$$V = \frac{kq}{d} + \frac{kq_2}{d_2} = \frac{4kq}{d}$$

From the second equation we get: $\frac{kq_2}{d_2} = \frac{3kq}{d}$, $q_2 = 3q \frac{d_2}{d} = 3qx$, where $x = \frac{d_2}{d}$.

Plugging this into the expression for energy we get $\frac{3q^2x}{d + d_2} = \frac{2q^2}{d}$, $\frac{3q^2x}{1+x} = 2q^2$,


$$\frac{3x}{1+x} = 2, \frac{3x}{1+x} = 2, x = \frac{d_2}{d} = 2. \text{ Thus } d_2 = 2d, q_2 = 3qx = +6q.$$

c) The field at the origin is: $E = \frac{kq}{d^2} - \frac{kq_2}{d_2^2} = \frac{kq}{d^2} \left(1 - \frac{6}{4}\right) = -\frac{kq}{2d^2}$.

As we can see the field direction is indeed in the negative x-direction.

PROBLEM 2. [20 points] – Light bulbs

The bulbs in the circuit are identical.

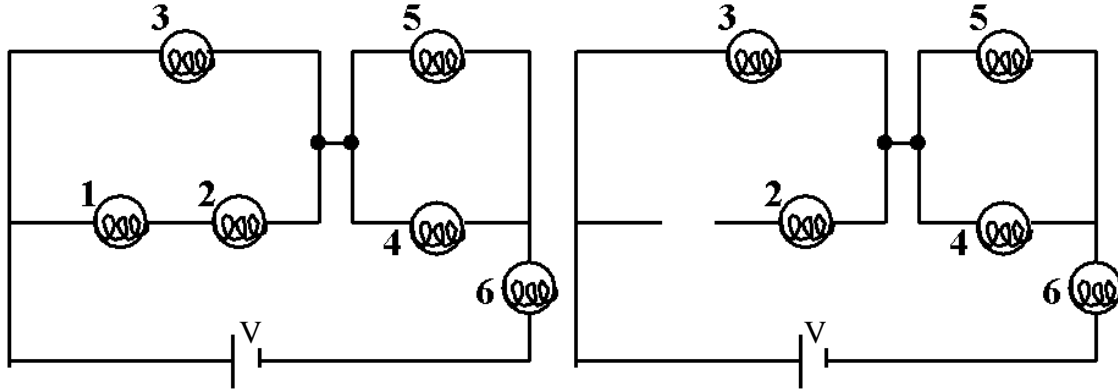

- (1) [6 points] In the circuit on the left, rank bulbs 1-6 in order of **decreasing** brightness. Briefly explain your answers.

Brightness of a bulb is determined by the power dissipated in the bulb and is given by I^2R . Since R is the same for all the bulbs, the current passing through the bulb determines the brightness of a bulb. The larger the current passing through the bulb, the brighter it will be.

If the current drawn from the battery is I , then bulb 6 sees the full current passing through it. Bulbs 4 and 5 are in parallel and have the same resistance, so they share this current and half of the current passes through each one of them. Bulbs 1 and 2 are in series with each other and parallel to bulb 3, thus the path through 2 and 3 has twice the resistance compared to the path with bulb 3. Therefore the current splits with two-thirds passing through bulb 3, while one-third of the current flows through bulbs 1 and 2.

Ordering the bulbs according to increasing current (or brightness) we get:

$$6 > 3 > 5 = 4 > 1 = 2$$

- (2) [6 points] If each bulb has a resistance of 12 ohms, what is the equivalent resistance of the circuit on the left?

$$\begin{aligned} R_{eq} &= R_6 + (R_5 // R_4) + (R_3 // (R_1 + R_2)) \\ &= R_6 + (R_5 * R_4) / (R_5 + R_4) + R_3 * (R_1 + R_2) / (R_1 + R_2 + R_3) \\ &= R + R/2 + 2R/3 \quad (\text{use the fact that all resistances are the same}) \\ &= 13R/6 = 13 * 12 / 6 \\ &= 26 \text{ Ohms.} \end{aligned}$$

(3) [8 points] When bulb 1 is removed, leaving a break in the circuit....

a) The brightness of bulb 3 _____

increases decreases stays the same

Briefly explain your answer:

When bulb 1 is removed all of the current now flows through 3, increasing its brightness

b) The brightness of bulb 6 _____

increases decreases stays the same

Briefly explain your answer:

The overall resistance of the circuit increases, therefore the current decreases, leading to a decreased brightness of bulb 6


PROBLEM 3 – 20 points

Three resistors are connected as shown in a circuit with a 12 volt battery. The resistances are:

For resistor A, $R_A = 4 \Omega$

For resistor B, $R_B = 3 \Omega$

For resistor C, R_C is an unknown value

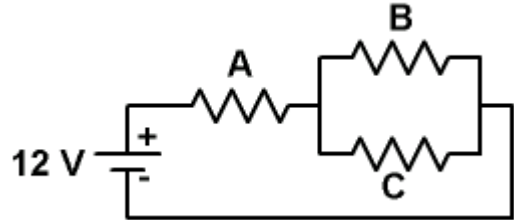

[3 points] (a) Which resistor has the most current passing through it?

A B C It depends on the value of R_C

Briefly justify your answer:

A gets all the current. The current then splits, with B getting some and C the rest.

[5 points] (b) Rank the resistors based on the potential difference across them, from largest to smallest.

$A > B > C$ $A > B = C$ $B > C > A$ $B = C > A$
 It depends on the value of R_C

Briefly justify your answer:

B and C have the same potential difference because they're in parallel. $V = IR$ for resistor A is bigger than that for B because A has both more current and more resistance.

[8 points] (c) If R_C , the resistance of resistor C, is increased, what happens to the currents through the different elements in the circuit?

i) The current through the battery: increases decreases stays the same

ii) The current through A: increases decreases stays the same

iii) The current through B: increases decreases stays the same

iv) The current through C: increases decreases stays the same

If the resistance of C increases the overall resistance of the circuit increases so the current is reduced. The current through the battery is the same as the current through A so they are both decreased. A now gets less voltage so the voltage across the B-C combination increases. Increasing the voltage across B increases B's current. The total current into the B-C combination has gone down, so if the current through B increases the current through C decreases.

[4 points] (d) If the current through the battery is 2.0 amps, what is R_C , the resistance of resistor C?

$R = V/I = 12/2 = 6$ ohms is the equivalent resistance of the circuit. This is the sum of A (4 ohms) and the B-C combination, so the B-C combination must be 2 ohms.

They're connected in parallel, so:

$$1/2 = 1/3 + 1/R_C, \text{ so } 1/R_C = 1/2 - 1/3 = 3/6 - 2/6 = 1/6$$

Therefore $R_C = 6$ ohms.